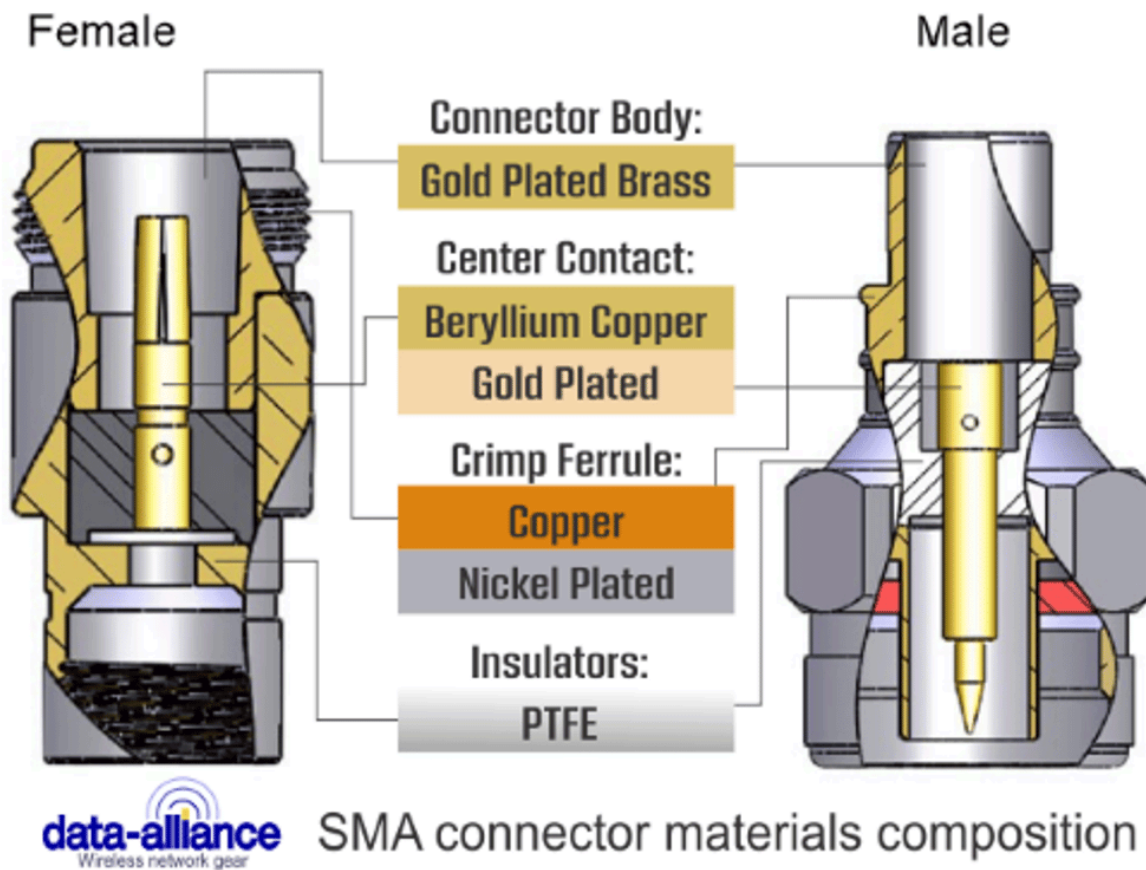


Lab 1

Practical Questions

1. cost of sma
 1. 18-24 for regular looking (digikey)
 2. ~40 for fancier (mcmaster carr)
2. mating plane
 1. horizontal or vertical mating, how it takes up space on a pcb / mount
3. SMA insulation



- 1.
2. not sure what the "shield" is referring to - there is electrical insulation (PTFE) to reduce noise from external RF signals that aren't traveling along the signal's metal bit. The rest of the cable bits seem to either be for strength or electrical shielding.
4. Field solver vs electrical simulator
 1. Field solver:
 1. Maxwell's equations from first principles
 2. Electrical Simulator
 1. using assumptions, just modeling current / voltage / capacitance / inductance using rules and abstractions from electromagnetic field - i.e higher order quantities using the various equivalents of ohms law (i.e. impedance versions for inductance and capacitance?) and differential equations.
5. What assumptions does LtSpice make during a DC simulation? Do capacitors matter?
 1. Ltspice uses currents - for no dynamics capacitors are opened circuits and capacitors are shorted. (stack exchange).
6. What assumptions does LtSpice make during an ac simulation?
 1. uses complex node voltages, linearizing all nonlinear devices.

7. What assumptions does LtSpice make during a transient simulation?
 1. Waveform compression - Tstep is not useful
8. 3 ways to damage RF equipment
 1. not following power ratings (always look at dBm!)
 2. DC (always ac couple through a capacitor and use low voltages to not spark across the airgap)
 3. physically breaking stuff (don't bend wire bc reflections are bad)

Theory Questions

1. What is the power dissipated in a 50 Ohm resistor (which is what most of our instruments look like) if it is driven by each of the following voltages? Express answers in both mW and dBm.

$$P = i^2 R = \frac{V^2}{R}$$

a.

1Vpp sinusoid with 0VDC offset

where R is the resistance, the average power for a cycle is

$$\frac{1}{2\pi R} \int_0^{2\pi} \sin(t)^2 dt$$

(dividing by 2π because we want the average power dissipation)

$$\begin{aligned}
 &= \frac{1}{2\pi R} \int_0^{2\pi} \frac{1 - \cos(2t)}{2} dt \\
 &= \frac{1}{4\pi R} (t + \sin(2t)) \Big|_0^{2\pi} \\
 &= \frac{1}{2R}
 \end{aligned}$$

At 50 Ohms, this is

$$\begin{aligned}
 \frac{1}{100} &= 10^{-2} \text{ W} \\
 &= 10 \text{ mW}
 \end{aligned}$$

in DMB this is

$$\begin{aligned}
 &10 \log_{10}(10) \\
 &= 10 \text{ dBm}
 \end{aligned}$$

b.

a 1Vpp sinusoid with 1VDC offset

Extrapolating from A:

$$\begin{aligned}
 &= \frac{1}{4\pi R} (3t + \sin(2t)) \Big|_0^{2\pi} \\
 &= \frac{3}{2R}
 \end{aligned}$$

Watts:

$$0.03 \text{ W} = 3 \text{ mW}$$

dBm:

$$10 \log_{10}(3) = 4.7 \text{ dBm}$$

c

a 1Vpp square wave with 0VDC offset

Assuming this goes from -0.5 V to 0.5V the average power is

$$\frac{0.5^2}{R} = \frac{1}{4R}$$

2:

Imagine 0dBm power is being dissipated in a load. First, express the load power in mW. Second, express the power level in dBm if the load power were multiplied by the following factors: 2x, 4x, 8x, 0.5x, 10x, 100x, 200x, 0.1x. Logarithmic math is your friend here, and this problem may go faster if you look for additive patterns in the results.

We know that

$$0dBm = 1mW.$$

For each of the factors (n) we have

$$10\log_{10}(n)$$


With logarithms we have the product rule, and can just do this easily (i.e. $\log_{10}(4) = \log_{10}(2) + \log_{10}(2)$)

We're just adding the logs of the factors (2 and 10 matter).


Multiplier/Power (mW)	Power (dbm)
1	0
2	3.
4	6
8	9
0.5	-3
10	10
100	20
200	23
0.1	-10

Lab

Circuit:

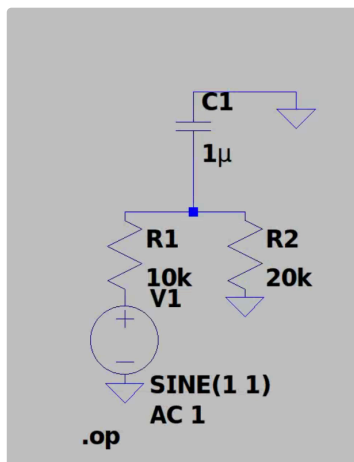


DC Operating point simulation:

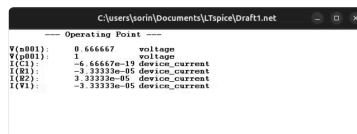


DC sweep of R2 (resistor connected to output and ground)

current:

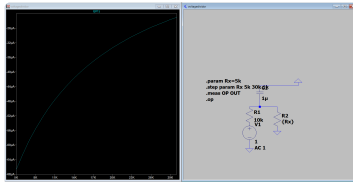


voltage:

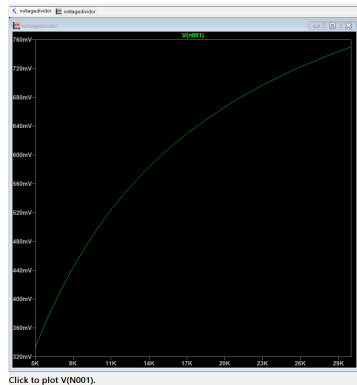

Click to plot V(N001).


vs desmos for a voltage divider
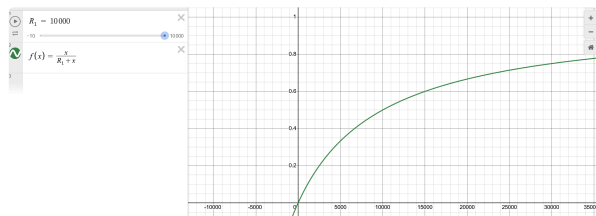
$$V_{\text{out}} = \frac{R_2}{R_1 + R_2} V_{\text{in}}$$



These look the same!

AC sweep around the corner frequency

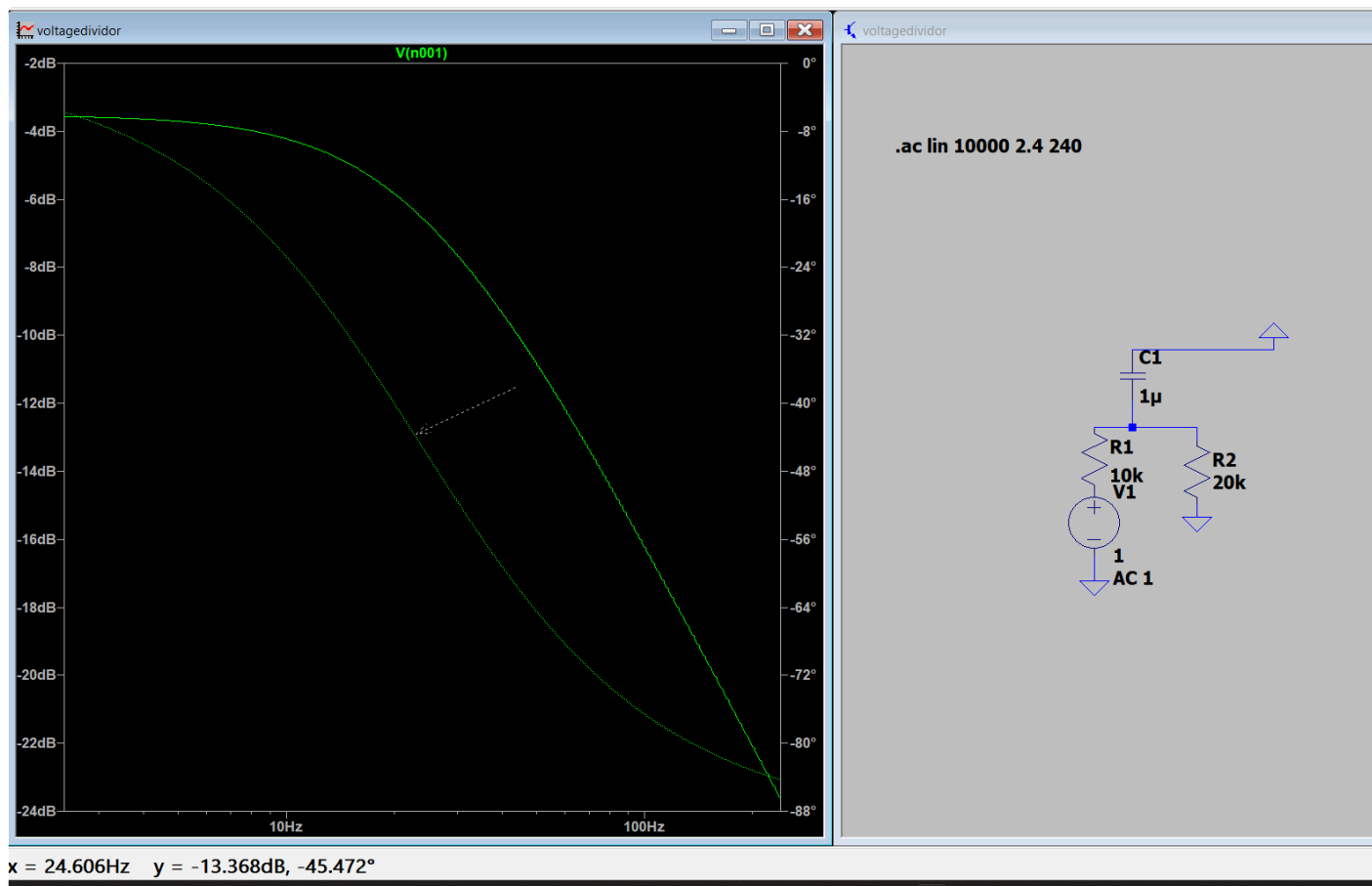

The corner frequency appears to be around 24 hz.

We can calculate this by writing out the impedance of each source, and finding the transfer function (which took way too long from dumb algebra errors):

The hand-drawn diagram shows a circuit with an AC voltage source V_{in} in series with a resistor R_1 . This is followed by a parallel combination of a capacitor C_s and a resistor R_2 . The output voltage is V_A .

$$I = \frac{V_{in}}{Z_{tot}}$$

$$Z_{tot} = R_1 + \left(\frac{1}{\frac{1}{R_2} + Cs} \right)$$

$$V_A = V_{in} - IR_1$$

We have

$$\begin{aligned}
 V_{\text{out}} &= V_{\text{in}} \left(1 - \frac{R_1}{R_1 + \frac{1}{\frac{1}{R_2} + cs}} \right) \\
 H &= 1 - \frac{\frac{R_1}{R_2} + R_1 cs}{\frac{R_1}{R_2} + R_1 cs + 1} \\
 &= 1 - \frac{\frac{R_1}{R_2} + R_1 cs}{R_1 CS + \left(\frac{R_1}{R_2} + 1 \right)} \\
 &= 1 - \frac{1}{\left(\frac{R_1}{R_2} + 1 \right)} \frac{\text{don't care}}{\frac{R_1 CS}{\frac{R_1}{R_2} + 1} + 1}
 \end{aligned}$$

(we don't care about the top for now - although because it has an S, I think this has a second corner frequency at half power? Its not second order because its not S^2 , its a zero instead of a pole. IDK, i didn't take E102).


We know that we have

$\frac{S}{\omega}$, so we get

$$\begin{aligned}
 2\pi f &= \frac{\frac{R_1}{R_2} + 1}{R_1 c} \\
 f &= \frac{\frac{R_1}{R_2} + 1}{2\pi R_1 c} \\
 &= 23.8 \text{ Hz}
 \end{aligned}$$

This agrees closely with what we found in the simulation (with large error from my arbitrary mouse position)


Full workthough on a whiteboard:

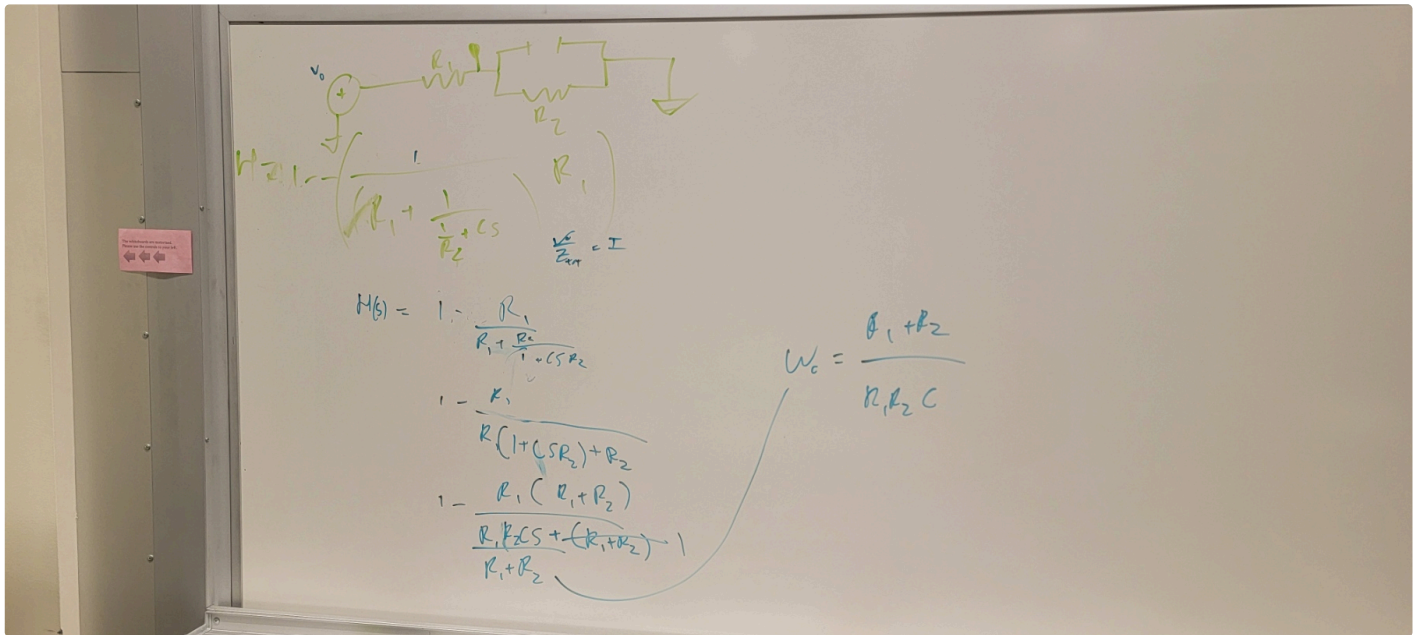

(I realized after I took the photo that I dropped a $(1 + CSR_2)$ in the numerator)

$$H(s) = \frac{R_1(R_1 + R_2)(1 + CSR_2)}{\frac{R_1 R_2 CS}{R_1 + R_2} + 1}$$

Transient of a step input in voltage

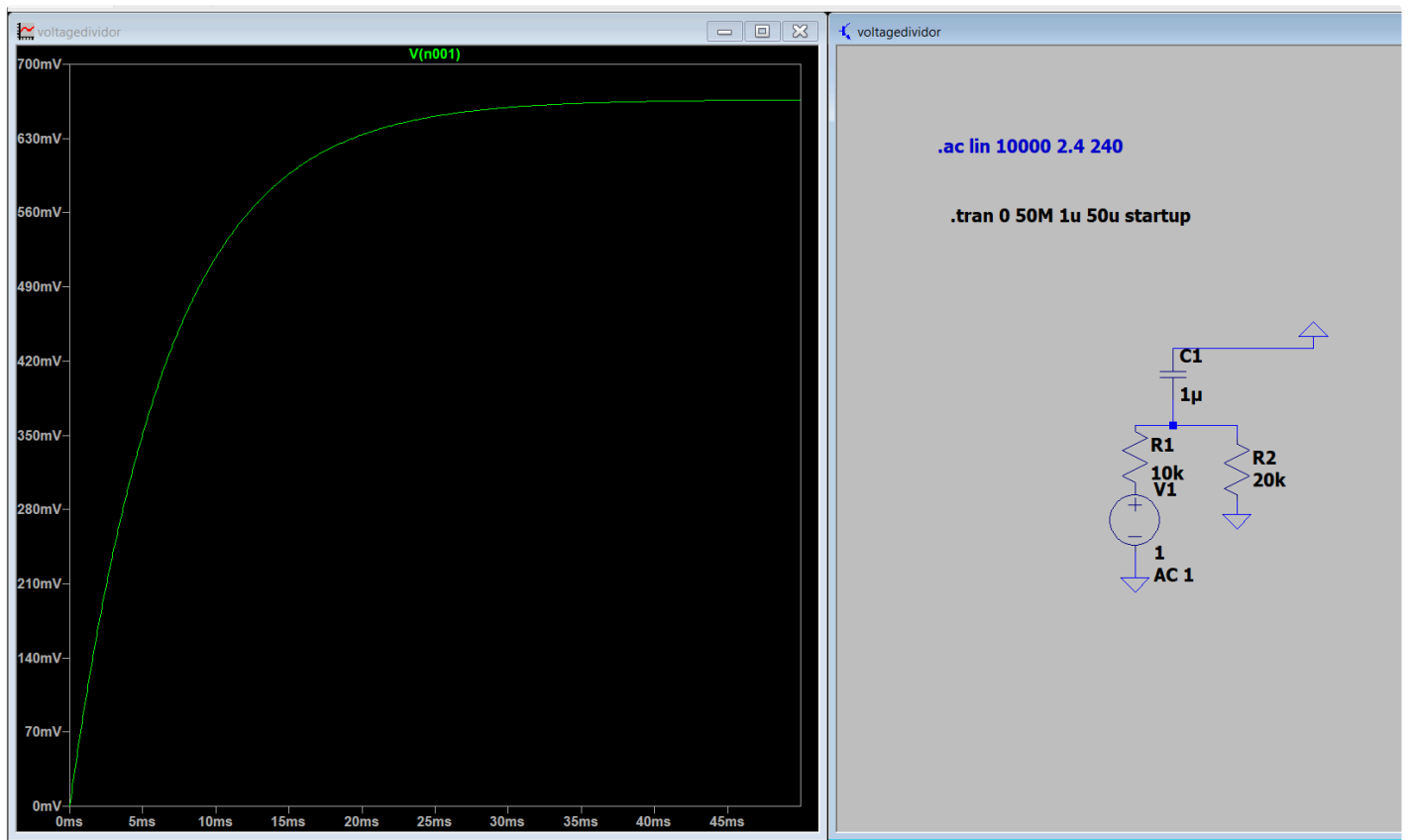

Because $\tau = \frac{1}{\omega_c}$, $= \tau \frac{1}{24 \cdot 2\pi} = 0.0067 = 6.7ms$

The actual one (in the simulation) is $\sim 666 * (1 - e^{-1}) = 421mv$, which happens at $6.7 ms$ ish. This is great!

EXTRA WORK BC I'M A DUMBASS AND FORGOT that $\tau = \frac{1}{\omega_c} s$ (and so derived it from scratch... I love being a physicist). Because we have the transfer function from before $H(s)$, we can get the rise time. We multiply the transfer functions of a step function $G(s)$ and our $H(s)$ to get the response to that step.

$$C(s) = G(s)H(s)$$

$$R(s) = \frac{1}{s}$$

So we have

$$\frac{1}{s} \frac{R_1(R_1 + R_2)(1 + CsR_2)}{\frac{R_1R_2CS}{R_1+R_2} + 1}$$

Lets call

$$\frac{R_1R_2C}{R_1+R_2} = \frac{1}{\omega_c}$$

this becomes

$$\begin{aligned} & \frac{R_1(R_1 + R_2)(1 + CsR_2)}{\frac{s^2}{\omega_c} + s} \\ &= \frac{R_1(R_1 + R_2)(1 + CsR_2)}{s(\frac{s}{\omega_c} + 1)} \end{aligned}$$

We can separate this with partial fractions

$$\frac{A}{S} + \frac{B}{\frac{s}{\omega_c} + 1}$$

$$\frac{As}{\omega_c} + Bs = CsR_2(R_1^2 + R_1R_2)$$

$$A = R_1(R_1 + R_2)$$

We can solve

$$\frac{R_1(R_1 + R_2)^2}{R_1R_2C} + Bs = CsR_2(R_1^2 + R_1R_2)$$

$$B = \frac{R_1R_2^2C^2(R_1^2 + R_1R_2)}{R_1(R_1 + R_2)^2}$$

Lets leave those as constants A and B because they're nasty AF. We can plug in numbers later.

$$C(s) = \frac{A}{s} + \frac{B}{\frac{s}{\omega_c} + 1}$$

$$= \frac{A}{s} + \frac{B\omega_c}{s + \omega_c}$$



This gets us

$$c(t) = A + B\omega_c e^{-\omega_c t}$$

This is where I remembered, at the end, that $\omega_c = \frac{1}{\tau}$. QED.

S Parameters

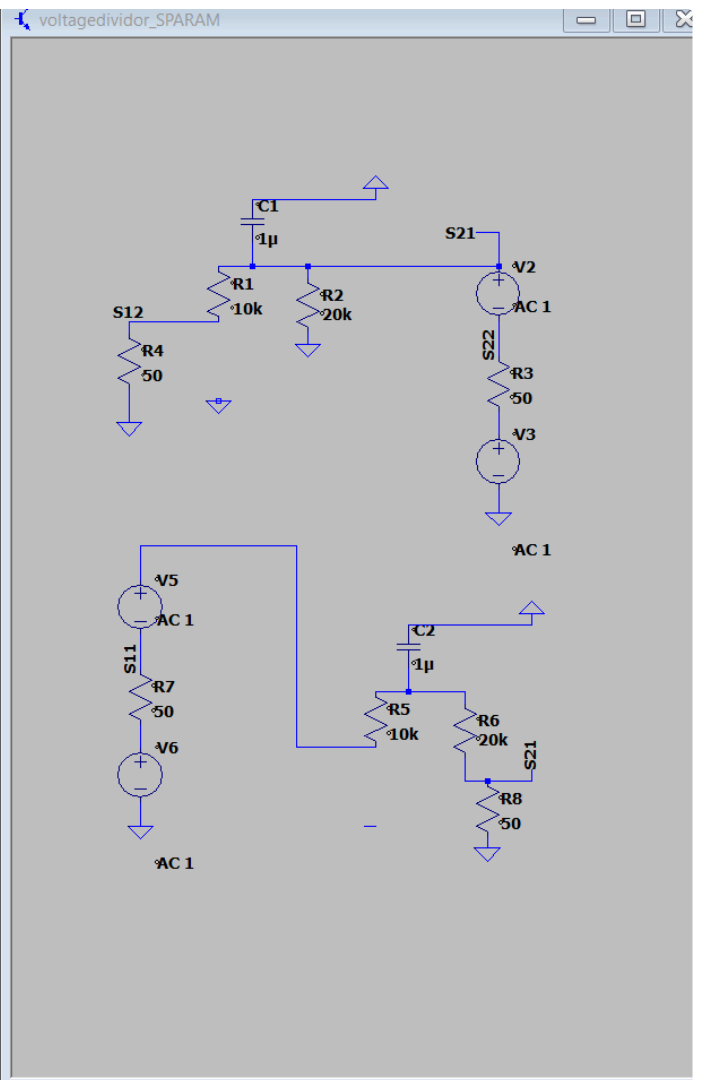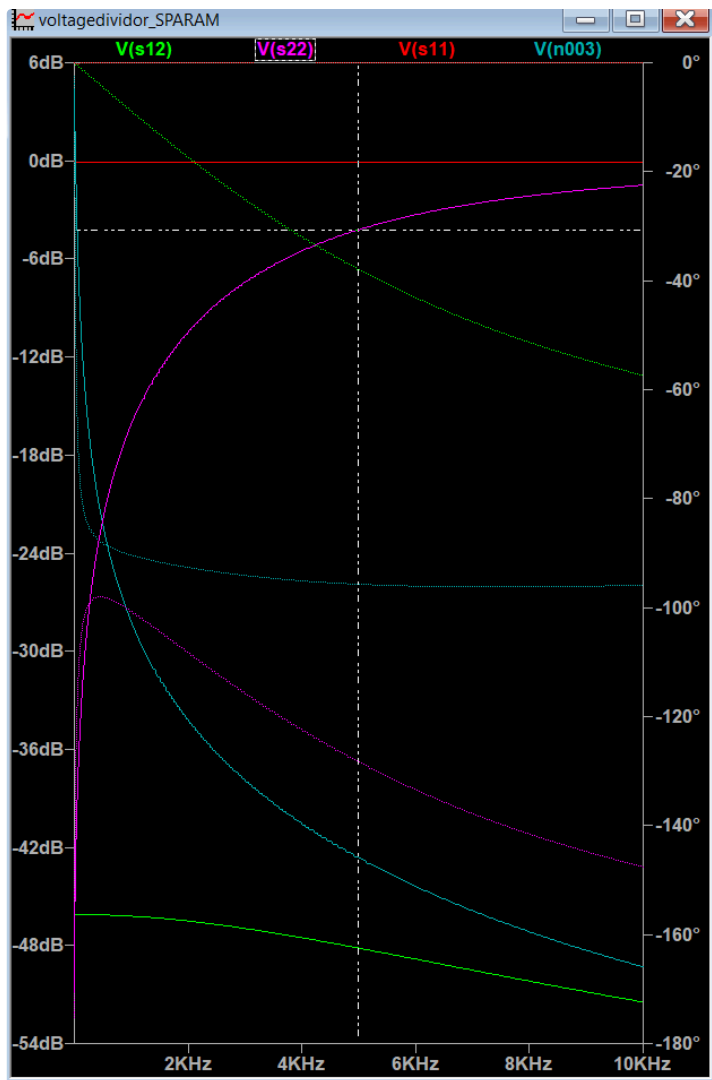S_{11} is always at 0dB, so I am not inclined to trust this. However, this is what I'm getting for following the tutorial found here:
<https://www.designers-guide.org/forum/Attachments/CreateS-ParameterSUBCKTinPSpice.pdf>



With 1 V DC on every voltage source (not sure why this should matter, but it does). Note different axis labels because behavior changed starkly ($f=10\text{k}$ vs 100k).

