

Op Amp Non-Idealities DC Challenges

Talks at a very nice speed. Awesome. Feels like Prof. Su for engineers.

Internally, op amps have tolerances - so even with the exact same input voltage there will still be minor differences $\neq$ railing out.

Lets look at a closed loop.

You can use superposition of voltages when the circuit is linear (no R, L, C) or active components, when there is at least one independent voltage/current source, and the op amp is in the linear region.

AWESOME ANSWERS TO MY QUESTION, I WANT THIS PERSON

In series, the larger impedance dominates.

In parallel, smaller dominates.